

GIT Department of Computer Engineering
CSE 232 - Spring 2020
Project 2

BARAN HASAN BOZDUMAN
171044036

CODE OF MULTIPLICATION

```
mult = 0;

while( a > 0 ){

    mult = mult + b;


    a = a - 1;

}
```


Its obvious the program does multiplication by using adding operations it makes a times add b to result.

DIAGRAM FOR DATAPATH

Firstly before we start to create circuit we need to create a data path and we do to changeable operations we connect them to mux and (for appropriate points for instance when you connect the wire which is you use often so you don't need to change it to one for each time) and if you assign something into a register after that state you compare it with something or change it to another value it behaves for old one so you need to put an empty statement between of them and it provides one more clock time.

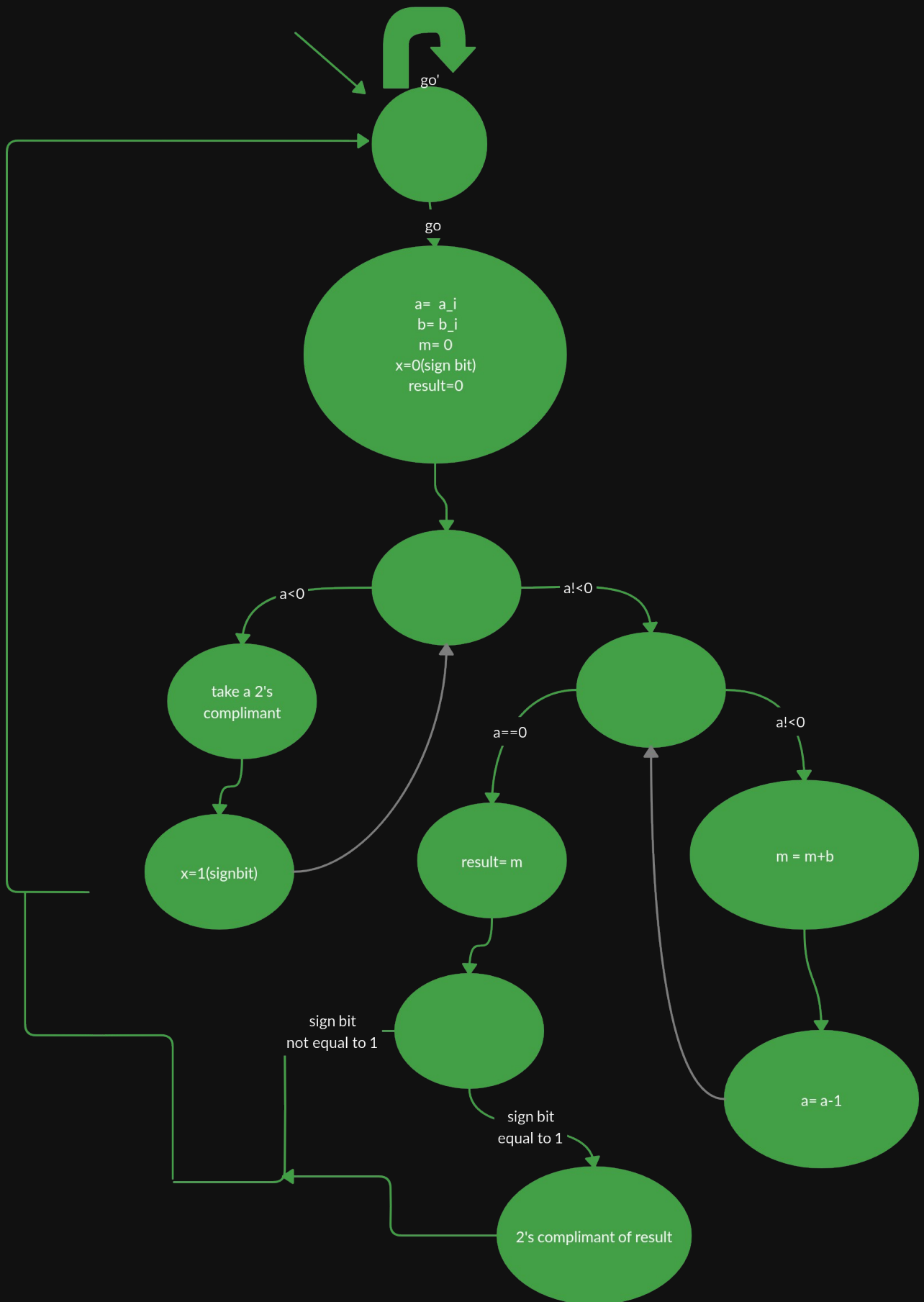

FINITE STATE MACHINE

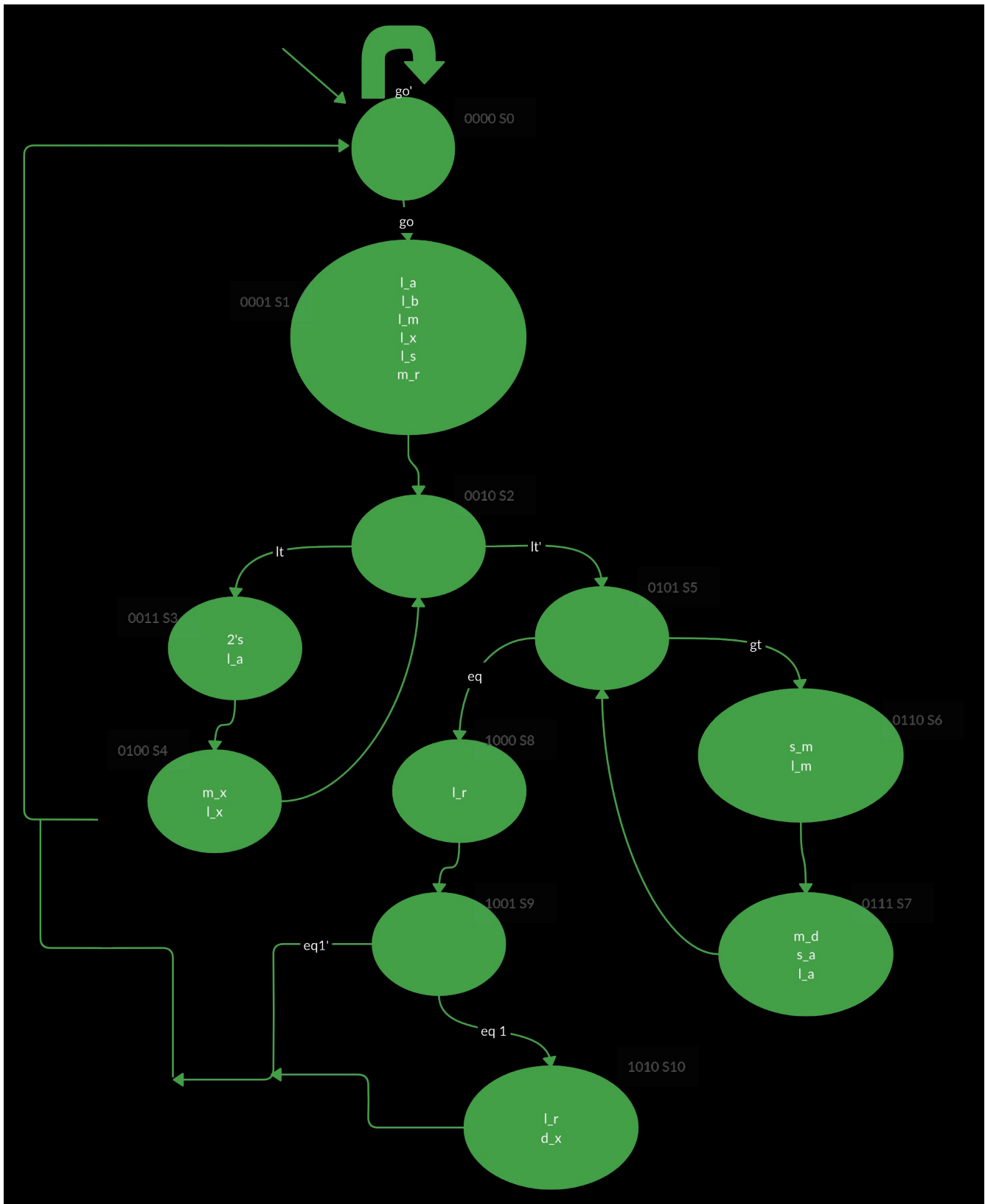

I convert our operationns into proper boolean values and we give name to our states I use *l_* for the load memory and *m_* is for the cahnge mux es *lt* (less than) *gt* (greater than) etc.

TRUTH TABLE
(for state changes)

INPUTS									OUTPUTS			
P3	P2	P1	P0	lt	eq	eq1	go	gr	N3	N2	N1	N0
0	0	0	0	-	-	-	0	-	0	0	0	0
0	0	0	0	-	-	-	1	-	0	0	0	1
0	0	0	1	-	-	-	-	-	0	0	1	0
0	0	1	0	1	-	-	-	-	0	0	1	1
0	0	1	0	0	-	-	-	-	0	1	0	1
0	0	1	1	-	-	-	-	-	0	1	0	0
0	1	0	0	-	-	-	-		0	0	1	0
0	1	0	1	-	-	-	-	1	0	1	1	0
0	1	0	1	-	1	-	-	-	1	0	0	0
0	1	1	0	-	-	-	-	-	0	1	1	1
0	1	1	1	-	-	-	-	-	0	1	0	1
1	0	0	0	-	-	-	-	-	1	0	0	1
1	0	0	1	-	-	1	-	-	1	0	1	0
1	0	0	1	-	-	0	-	-	0	0	0	0
1	0	1	0	-	-	-	-	-	0	0	0	0

$N3 = P3'P2P1'P0eq + P3P2'P1'P0' + P3P2'P1'P0eq1$
 simplified = $P3P2'P1'(P0 + P0eq1) + P3'P2P1'P0eq$
 $(P0' + eq)$

$N2 = P3'P2'P1P0'lt' + P3'P2'P1P0 + P3'P2P1'P0gr + P3'P2P1P0' + P3'P2'P1P0$
 simplified = $P3'P1P0 + P3'P1lt' + P3'P1P2 + P3'P2P0gr$

$N1 = P3'P2'P1'P0 + P3'P2'P1P0'lt + P3'P2P1'P0' + P3'P2P1'P0gr + P3'P2P1P0' + P3P2'P1'P0eq1$
 simplified = $P3'P1P0'lt + P3'P2'P1'P0 + P3'P2P1'gr + P3'P2P0' + P0P1'P2'eq1$

$N0 = P3'P2'P1'P0'go + P3'P2'P1P0'lt + P3'P2'P1P0'LT' + P3'P2P1P0' + P3'P2P1P0 + P3P2'P1'P0'$
 simplified = $P3P2'P1'P0' + P3'P1P0' + P3'P2P1 + P2'P1'P0'go$

TRUTH TABLE
(for state operations)

INPUTS					OUTOUTS										
	P3	P2	P1	P0	la	lb	lm	lx	dx	2s	lr	mx	sm	md	sa
S0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
S1	0	0	0	1	1	1	1	1	0	0	0	0	0	0	0
S2	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
S3	0	0	1	1	1	0	0	0	0	0	0	0	0	0	0
S4	0	1	0	0	0	0	0	1	0	0	0	1	0	0	0
S5	0	1	0	1	0	0	0	0	0	0	0	0	0	0	0
S6	0	1	1	0	0	0	1	0	0	0	0	0	1	0	0
S7	0	1	1	1	1	0	0	0	0	0	0	0	0	1	1
S8	1	0	0	0	0	0	0	0	0	0	1	0	0	0	0
S9	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0
S10	1	0	1	0	0	0	0	0	1	0	0	0	0	0	0

La =S1 +S3 +S7

lb =S1

lm = S1 +S6

lx =S1 +S4

dx =S10

2s =S3

lr = S8 +S10

mx = S4

sm = S6

md =S7

sa =S7

mr =S1

note: My logisim circuit is working for negative numbers two just may be it will be give an overflow error if the number bigger than 16 bit but as teacher indicated it does not matter..